

Total No. of Questions : 8]

SEAT No. :

P1720

[5058]-353

[Total No. of Pages : 4

**T.E.(Electronics.)
NETWORK SYNTHESIS
(2012 Pattern)(Semester-I)**

Time : 2½Hours]

[Max. Marks : 70

Instructions to the candidates:

- 1) Answer Q1 or Q2, Q3 or Q4, Q5 or Q6, Q7 or Q8.
- 2) Neat diagrams must be drawn wherever necessary.
- 3) Figures to the right side indicate full marks
- 4) Use of electronic pocket calculator is allowed.
- 5) Assume suitable data if necessary.

Q1) a) Test whether the following functions are positive real, **[6]**

i)
$$F(s) = \frac{s^2 + 4}{2s^3 + 3s^2 + 6s + 1}$$

ii)
$$F(s) = \frac{(s+2)(s+4)}{(s+1)(s+3)}$$

b) Synthesize the following function using cauer-I and cauer-II form, **[6]**

$$Z(s) = \frac{2(s+1)(s+3)}{s(s+2)}$$

c) State the properties of Transfer function and synthesize the following Transfer function. **[8]**

$$Z_{21}(s) = \frac{s}{s^3 + 3s^2 + 3s + 2}$$

as a 1Ω terminated two port LC ladder network.

OR

P.T.O.

Q2) a) Define all the four transfer functions for a two port network and explain effect of location of poles and zeros on response of the network. [7]

b) State and explain the properties of LC impedance function and also indicate which of the following functions are LC, RC, RL, or RLC impedance functions. [7]

i) $Z(s) = \frac{s^3 + 2s}{s^4 + 3s^2 + 2}$

ii) $Z(s) = \frac{s^2 + 4s + 3}{s^2 + 6s + 8}$

iii) $Z(s) = \frac{s^4 + 4s^2 + 3}{s^3 + 2s}$

c) Define constant resistance network? Design a bridge T network terminated in 1Ω to give a voltage transfer ratio [6]

$$G_{12}(s) = \frac{s+2}{s+3}$$

Q3) a) Compare Butterworth and Chebyshev Approximation Techniques. [4]

b) Determine the transfer function and realize low pass Butterworth approximation filter whose requirements are characterized by,

Pass band edge frequency 0.2 Mrad/sec, maximum loss in pass band 2dB, stop band loss at least 60 dB at 6Mrad/sec [8]

c) Normalized third order Low pass filter is shown below in Fig.1 [4]

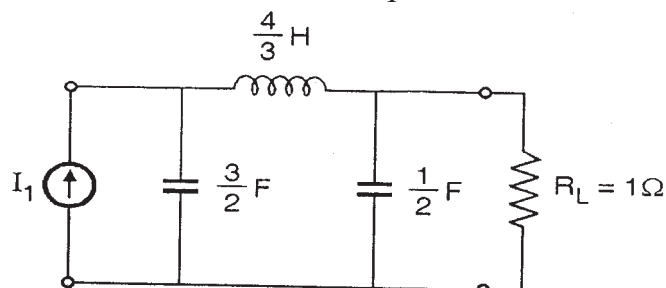


Figure 1

Design the corresponding high pass filter with its cutoff frequency $\omega_c = 10^4 \text{ rad/sec}$ and the impedance load of 500Ω

OR

- Q4)** a) Explain frequency and impedance Scaling. [4]
 b) State the properties of Butterworth Approximation. [4]
 c) Determine the transfer function of Chebyshev low pass filter to meet the following specification, [8]
 i) 0.5 dB ripple in the pass band.
 ii) Cut off frequency $\omega_c = 5 \times 10^5$ rad/sec.
 iii) The Magnitude must be down to 30 dB at $\omega = 1.5 \times 10^6$ rad/sec.
 iv) Load resistance = 600Ω
- Q5)** a) Differentiate between Passive and Active filters. [4]
 b) Synthesize 2nd order active low pass filter to have a pole frequency of 2 kHz and pole Q of 10. Then using RC-CR transformation, realize HPF with same cut off frequency. [6]
 c) What are the advantages and disadvantages of biquad topologies of Active filter? [6]

OR

- Q6)** a) Design 2nd order Sallen and Key high pass Butterworth filter having cut off frequency of 600 Hz. [4]
 b) Explain the different feedback topologies used in active filter designing. [4]
 c) Synthesize the following high pass filter function using RC-CR transformation. [8]

$$H(s) = \frac{ks^2}{s^2 + s + 25}$$

- Q7)** a) Define Sensitivity? Give some of its important properties. [4]
 b) Explain the concept of gain sensitivity? Also explain the various factors affecting the gain sensitivity. [6]
 c) Explain effect of the following op-amp characteristics on the active filter. [8]
 i) Dynamic range
 ii) Input Bias Current.
 iii) Slew rate.
 iv) CMRR

OR

- Q8) a)** For the series RLC circuit shown in Fig.2, find transfer function V_2/V_1 . Calculate the sensitivities of K, the pole frequency ω_p , the factor(Q_p) with respect to R,L and C. Comment on the result obtained. [6]

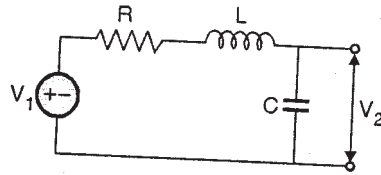


Figure 2

- b)** Prove the following sensitivity relationships. [6]

i) $S_x^{p^n} = nS_x^p$

ii) $S_{\sqrt{x}}^p = 2S_x^p$

iii) $S_x^{y+c} = \frac{y}{y+c} S_x^y$

- c)** Explain the effect of offset voltage on active filter performance. The input to the inverter shown in Fig.3 is a sine wave of amplitude 5 volt. If the slew rate of the op amp is $1\text{V}/\mu\text{sec}$, find the frequency at which the slew rate limiting occurs. [6]

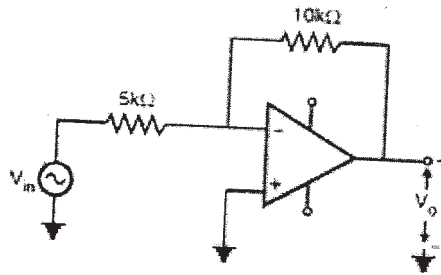


Figure 3

