

Total No. of Questions—8]

[Total No. of Printed Pages—3

Seat No.	
-------------	--

**[5057]-272**

**S.E. (Instrumentation and Control Engineering) (I Sem.)**

**EXAMINATION, 2016**

**LINEAR INTEGRATED CIRCUITS**

**(2012 PATTERN)**

**Time : Two Hours**

**Maximum Marks : 50**

**N.B. :—** (i) Solve Q. No. 1 or Q. No. 2, Q. No. 3 or Q. No. 4,  
Q. No. 5 or Q. No. 6, Q. No. 7 or Q. No. 8.

(ii) Neat diagrams must be drawn wherever necessary.

(iii) Figures to the right indicate full marks.

(iv) Your answers will be valued as a whole.

(v) Use of logarithmic tables, slide rule, Mollier charts, electronic pocket calculator and steam tables is allowed.

(vi) Assume suitable data, if necessary.

1. (a) Explain the difference between open-loop and closed-loop OP-AMP with neat diagrams. [6]
- (b) Explain different types of Noise in OP-AMP. [6]

*Or*

2. (a) How to measure the Common Mode Rejection Ratio of OP-AMP with neat circuit diagrams ? [6]

P.T.O.

- (b) Derive the voltage equation for the voltage-series feedback amplifier with neat circuit diagram. [6]
3. (a) Explain chopper stabilized amplifier with neat circuit diagram. [6]
- (b) State Barkhausen criteria for suitable oscillation. Design Wein-bridge oscillator for the output frequency of  $F_o = 1 \text{ kHz}$  with neat circuit diagram. Assume suitable data. [6]

*Or*

4. (a) Explain current booster circuit using OP-AMP with neat diagrams. [6]
- (b) Explain Inverting Schmitt trigger with neat circuit diagram, waveforms and hysteresis. [6]
5. (a) Explain Astable Multivibrator using IC 555 with neat circuit diagram and waveforms. [8]
- (b) Draw and Design High Voltage Regulator (HVR) using IC 723 for 12 V output. Assume suitable data. [5]

*Or*

6. (a) Design One-shot multivibrator using IC 555 with neat circuit diagrams for the pulse width of 2.97 ms. [5]

- (b) What is Regulator ? State advantages of switching regulator over linear regulators. [8]
7. (a) Explain second order Butterworth high-pass filter and also draw circuit diagram. [8]
- (b) What is “Q” of filter ? Draw a detailed ideal and practical responses for all types of filters. [5]

*Or*

8. (a) Explain Butterworth Twin-T filter using neat circuit diagram and its response. [6]
- (b) Design first order Butterworth non-inverting low-pass filter for the cut-off frequency of 1000 Hz. Assume suitable data with neat circuit diagrams. [7]